

VLSI Lab Report

Submitted by:

Name: Sourav Dutta

Roll: 001610501076

Group: A3

Department of Computer Science and Engineering (BCSE-4)
Jadavpur University, Kolkata

CONTENTS

S.No.		Page
1.	Design a 4x2 Encoder	3
2.	Design a 8x3 Encoder	6
3.	Design a decimal-to-BCD Encoder	8
4.	Design a 1x2 Decoder	10
5.	Design a 2x4 Decoder	13
6.	Design a 3x8 Decoder	16

ASSIGNMENT – 1

Problem

Design a 4x2 Encoder using
(a) Structural modelling
(b) Behavioural modelling


Description

An **Encoder** is a combinational circuit that performs the reverse operation of Decoder. It has maximum of 2^n input lines and 'n' output lines. It will produce a binary code equivalent to the input, which is active High. Therefore, the encoder encodes 2^n input lines with 'n' bits. It is optional to represent the enable signal in encoders. Here, the value of n is 2, as there are 4 input lines and 2 output lines.

Truth Table

Input				Output	
i_3	i_2	i_1	i_0	o_1	o_0
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1

Block Diagram

 

VHDL Code

i) Using structural modelling

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity fourtotwoencoder_structural is
    Port ( i : in  STD_LOGIC_VECTOR (3 downto 0);
           o : out STD_LOGIC_VECTOR (1 downto 0));
end fourtotwoencoder_structural;

architecture Structural of fourtotwoencoder_structural is
begin

    o(0)<=i(1) or i(3);
    o(1)<=i(2) or i(3);

end Structural;
```

ii) Using behavioral modelling (using concurrent statements)

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity fourtotwoencoder_behavioral_c is
    Port ( i : in  STD_LOGIC_VECTOR (3 downto 0);
           o : out STD_LOGIC_VECTOR (1 downto 0));
end fourtotwoencoder_behavioral_c;

architecture Behavioral of fourtotwoencoder_behavioral_c is
begin

with i select o<=
    "00" when "0001",
    "01" when "0010",
    "10" when "0100",
    "11" when "1000",
    "ZZ" when others;

end Behavioral;
```

iii) Using behavioural modelling (using sequential statements)

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity fourtotwoencoder_behavioral_s is
    Port ( i : in  STD_LOGIC_VECTOR (3 downto 0);
           o : out STD_LOGIC_VECTOR (1 downto 0));
end fourtotwoencoder_behavioral_s;
```

```
architecture Behavioral of fourtotwoencoder_behavioral_s is
begin

Process(i)
begin
    case i is
        when "0001" => o<="00";
        when "0010" => o<="01";
        when "0100" => o<="10";
        when "1000" => o<="11";
        when others => o<="ZZ";
    end case;

end Process;

end Behavioral;
```

ASSIGNMENT – 2

Problem

Design a 8x3 Encoder using

- (a) Select statement
- (b) Case statement


Description

An **Encoder** is a combinational circuit that performs the reverse operation of Decoder. It has maximum of 2^n input lines and 'n' output lines. It will produce a binary code equivalent to the input, which is active High. Therefore, the encoder encodes 2^n input lines with 'n' bits. It is optional to represent the enable signal in encoders. Here, the value of n is 3, as there are 8 input lines and 3 output lines.

Truth Table

Input								Output		
i_7	i_6	i_5	i_4	i_3	i_2	i_1	i_0	o_2	o_1	o_0
0	0	0	0	0	0	0	1	0	0	0
0	0	0	0	0	0	1	0	0	0	1
0	0	0	0	0	1	0	0	0	1	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	0
0	0	1	0	0	0	0	0	1	0	1
0	1	0	0	0	0	0	0	1	1	0
1	0	0	0	0	0	0	0	1	1	1

Block Diagram

 

VHDL Code

i) Using select statements (behavioural modelling)

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity eighttothree_select is
    Port ( i : in  STD_LOGIC_VECTOR (7 downto 0);
          o : out  STD_LOGIC_VECTOR (2 downto 0));
end eighttothree_select;

architecture Behavioral of eighttothree_select is
begin

with i select o<=
    "000" when "00000001",
    "001" when "00000010",
    "010" when "00000100",
    "011" when "00001000",
    "100" when "00010000",
    "101" when "00100000",
    "110" when "01000000",
    "111" when "10000000",
    "ZZZ" when others;

end Behavioral;
```

ii) Using case statements (behavioural modelling)

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity eighttothreeee_case is
    Port ( i : in  STD_LOGIC_VECTOR (7 downto 0);
          o : out  STD_LOGIC_VECTOR (2 downto 0));
end eighttothreeee_case;

architecture Behavioral of eighttothreeee_case is
begin

Process(i)
begin
    case i is
        when "00000001" => o<="000";
        when "00000010" => o<="001";
        when "00000100" => o<="010";
        when "00001000" => o<="011";
        when "00010000" => o<="100";
        when "00100000" => o<="101";
        when "01000000" => o<="110";
        when "10000000" => o<="111";
        when others => o<="ZZZ";
    end case;
end Process;

end Behavioral;
```

ASSIGNMENT – 3

Problem

Design a Decimal-to-BCD Encoder.


Description

An **Encoder** is a combinational circuit that performs the reverse operation of Decoder. It has maximum of 2^n input lines and 'n' output lines. It will produce a binary code equivalent to the input, which is active High. Therefore, the encoder encodes 2^n input lines with 'n' bits. It is optional to represent the enable signal in encoders. Here, the Decimal-to-BCD encoder has 10 input lines and 4 output lines.

Truth Table

Input										Output			
i_9	i_8	i_7	i_6	i_5	i_4	i_3	i_2	i_1	i_0	o_3	o_2	o_1	o_0
0	0	0	0	0	0	0	0	0	1	0	0	0	0
0	0	0	0	0	0	0	0	1	0	0	0	0	1
0	0	0	0	0	0	0	1	0	0	0	0	1	0
0	0	0	0	0	0	1	0	0	0	0	0	1	1
0	0	0	0	0	1	0	0	0	0	0	1	0	0
0	0	0	0	1	0	0	0	0	0	0	1	0	1
0	0	0	1	0	0	0	0	0	0	0	1	1	0
0	0	1	0	0	0	0	0	0	0	0	1	1	1
0	1	0	0	0	0	0	0	0	0	1	0	0	0
1	0	0	0	0	0	0	0	0	0	1	0	0	1

Block Diagram

 

VHDL Code

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity decimaltoBCD_structural is
    Port ( i : in  STD_LOGIC_VECTOR (9 downto 0);
          o : out  STD_LOGIC_VECTOR (3 downto 0));
end decimaltoBCD_structural;

architecture Structural of decimaltoBCD_structural is
begin
    o(3) <= i(9) or i(8);
    o(2) <= i(7) or i(6) or i(5) or i(4);
    o(1) <= i(7) or i(6) or i(3) or i(2);
    o(0) <= i(9) or i(7) or i(5) or i(3) or i(1);

end Structural;
```

ASSIGNMENT – 4

Problem

Design a 1x2 Decoder using

- (a) Structural design
- (b) Sequential statement
- (c) Concurrent statement


Description

Decoder is a combinational circuit that has 'n' input lines and maximum of 2^n output lines. One of these outputs will be active High based on the combination of inputs present, when the decoder is enabled. That means decoder detects a particular code. The outputs of the decoder are nothing but the **min terms** of 'n' input variables lines, when it is enabled. Here, the value of n is 1, as there are 1 input lines and 2 output lines.

Truth Table

Input		Output	
e	i ₀	o ₁	o ₀
0	x	0	0
1	0	0	1
1	1	1	0

Block Diagram

 

VHDL Code

i) Using structural design

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity onetotwodecoder_structural is
    Port ( i : in  STD_LOGIC_VECTOR (3 downto 0);
          o : out STD_LOGIC_VECTOR (1 downto 0));
end onetotwodecoder_structural;

architecture Structural of fourtotwoencoder_structural is
begin

    o(0)<= e and not(i);
    o(1)<= e and i;

end Structural;
```

ii) Using sequential statements (behavioural modelling)

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity onetotwodecoder_seq is
    Port ( e : in  STD_LOGIC;
          i : in  STD_LOGIC;
          o : out STD_LOGIC_VECTOR (1 downto 0));
end onetotwodecoder_seq;

architecture Behavioral of onetotwodecoder_seq is
begin

process(e,i)
begin

    if(e='0') then
        o<="00";
    elsif(i='0') then
        o<="01";
    elsif(i='1') then
        o<="10";
    end if;

end process;
end Behavioral;
```

iii) Using concurrent statements (behavioural modelling)

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
```

```
entity onetotwodecoder_con is
    Port ( e : in  BIT;
           i : in  BIT;
           o : out BIT_VECTOR (1 downto 0));
end onetotwodecoder2;

architecture Behavioral of onetotwodecoder2 is
begin
    with (e & i) select o<=
        "01" when "10",
        "10" when "11",
        "00" when others;
end Behavioral;
```

ASSIGNMENT – 5

Problem

Design a 2x4 Decoder using

- (a) Structural design
- (b) Sequential statement
- (c) Concurrent statement


Description

Decoder is a combinational circuit that has 'n' input lines and maximum of 2^n output lines. One of these outputs will be active High based on the combination of inputs present, when the decoder is enabled. That means decoder detects a particular code. The outputs of the decoder are nothing but the **min terms** of 'n' input variables lines, when it is enabled. Here, the value of n is 2, as there are 2 input lines and 4 output lines.

Truth Table

Input			Output			
e	i ₁	i ₀	o ₃	o ₂	o ₁	o ₀
0	x	x	0	0	0	0
1	0	0	0	0	0	1
1	0	1	0	0	1	0
1	1	0	0	1	0	0
1	1	1	1	0	0	0

Block Diagram

 

VHDL Code

i) Using structural design

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity twotofourdecoder is
    Port ( e : in  BIT;
          i : in  BIT_VECTOR (1 downto 0);
          o : out BIT_VECTOR (3 downto 0));
end twotofourdecoder;

architecture Structural of twotofourdecoder is
begin

    o(0)<= e and not(i(1)) and not (i(0));
    o(1)<= e and not(i(1)) and (i(0));
    o(2)<= e and(i(1)) and not (i(0));
    o(3)<= e and (i(1)) and (i(0));

end Structural;
```

ii) Using sequential statements (behavioural modelling)

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity twotofourdecoder_seq is
    Port ( e : in  STD_LOGIC;
          i : in  STD_LOGIC_VECTOR (1 downto 0);
          o : out  STD_LOGIC_VECTOR (3 downto 0));
end twotofourdecoder_seq;

architecture Behavioral of twotofourdecoder_seq is
begin

    process(e,i)
    begin

        if(e='0') then
            o<="0000";
        elsif(i="00") then
            o<="0001";
        elsif(i="01") then
            o<="0010";
        elsif(i="10") then
            o<="0100";
        elsif(i="11") then
            o<="1000";
        end if;
    end process;
end Behavioral;
```

iii) Using concurrent statements (behavioural modelling)

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity twotofourdecoder_co is
    Port ( e : in  STD_LOGIC;
           i : in  STD_LOGIC_VECTOR (1 downto 0);
           o : out STD_LOGIC_VECTOR (3 downto 0));
end twotofourdecoder_co;

architecture Behavioral of twotofourdecoder_co is
begin

    with (e & i) select o<=
        "0001" when "100",
        "0010" when "101",
        "0100" when "110",
        "1000" when "111",
        "0000" when others;

end Behavioral;
```

ASSIGNMENT – 6

Problem

Design a 3x8 Decoder

- (a) By component instantiate
- (b) By using procedural statement


Description

Decoder is a combinational circuit that has 'n' input lines and maximum of 2^n output lines. One of these outputs will be active High based on the combination of inputs present, when the decoder is enabled. That means decoder detects a particular code. The outputs of the decoder are nothing but the **min terms** of 'n' input variables lines, when it is enabled. Here, the value of n is 3, as there are 3 input lines and 8 output lines.

Truth Table

Input				Output							
e	i ₂	i ₁	i ₀	o ₇	o ₆	o ₅	o ₄	o ₃	o ₂	o ₁	o ₀
0	x	x	x	0	0	0	0	0	0	0	0
1	0	0	0	0	0	0	0	0	0	0	1
1	0	0	1	0	0	0	0	0	0	1	0
1	0	1	0	0	0	0	0	0	1	0	0
1	0	1	1	0	0	0	0	1	0	0	0
1	1	0	0	0	0	0	1	0	0	0	0
1	1	0	1	0	0	1	0	0	0	0	0
1	1	1	0	0	1	0	0	0	0	0	0
1	1	1	1	1	0	0	0	0	0	0	0

Block Diagram

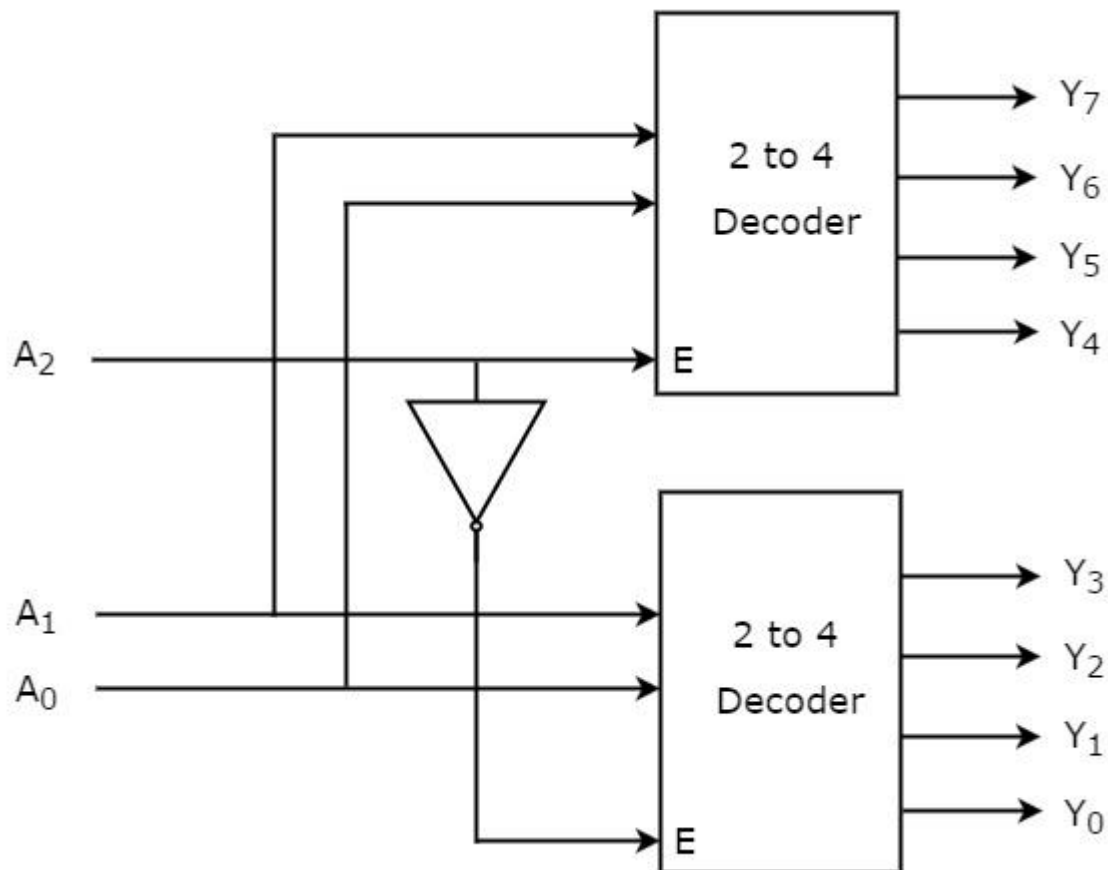

VHDL Code

i) By component instantiate

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity threeto8dec_comp is
    Port ( inp : in  STD_LOGIC_VECTOR (2 downto 0);
          en  : in  STD_LOGIC;
          op  : out STD_LOGIC_VECTOR (7 downto 0));
end threeto8dec_comp;

architecture Behavioral of threeto8dec_comp is

    component twotofourdecoder is
        Port ( e : in  STD_LOGIC;
              i : in  STD_LOGIC_VECTOR (1 downto 0);
              o : out STD_LOGIC_VECTOR (3 downto 0));
    end component;

    signal notinp:STD_LOGIC;
begin
    notinp <= not inp(2);
    dec1:twotofourdecoder port map(inp(2),inp(1 downto 0),op(7 downto 4));
    dec2:twotofourdecoder port map(notinp,inp(1 downto 0),op(3 downto 0));
end Behavioral;
    
```

ii) By using procedural statement

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity threeto8dec_proc is
    Port ( inp : in  STD_LOGIC_VECTOR (2 downto 0);
          op  : out STD_LOGIC_VECTOR (7 downto 0));
end threeto8dec_proc;
architecture Behavioral of threeto8dec_proc is

    procedure twotofourdecoder ( e : in  STD_LOGIC;
                                i : in  STD_LOGIC_VECTOR (1 downto 0);
                                o : out STD_LOGIC_VECTOR (3 downto 0)) is

    begin

        with (e & i) select o:=
            "0001" when "100",
            "0010" when "101",
            "0100" when "110",
            "1000" when "111",
            "0000" when others;

    end procedure;

    begin

        process(inp)
            variable varop:STD_LOGIC_VECTOR (7 downto 0);
            begin
                dec1:twotofourdecoder(inp(2),inp(1 downto 0),varop(7 downto 4));
                dec2:twotofourdecoder(not inp(2),inp(1 downto 0),varop(3 downto
0));
                op<=varop;
            end process;

        end Behavioral;
```